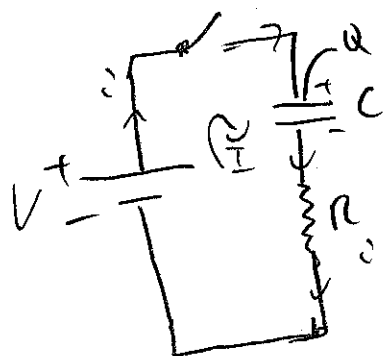


# RC - Circuits

①

## (a) DC series circuit



$Q(0) = 0$  at  $t=0$  switch closed

$$\textcircled{1} -V + \frac{Q}{C} + Ri = 0$$

$i = + \frac{dQ}{dt} = \dot{Q}$  (+, because current flows towards the positive plate)

$$\dot{Q} + \frac{1}{RC} Q = \frac{V}{R}$$

$\Rightarrow$  General solution of hom. eq.

$$\dot{Q} = -\frac{1}{RC} Q \Rightarrow \frac{dQ}{Q} = -\frac{dt}{RC}$$

$$\Rightarrow \ln\left(\frac{Q}{A}\right) = -\frac{t}{RC} \Rightarrow Q(t) = A \exp\left(-\frac{t}{RC}\right)$$

Particular solution of inhom. eq.

$Q = A_1 = \text{const}$  (ansatz of type of rhs of equation)

$$\Rightarrow \frac{A_1}{RC} = \frac{V}{R} \Rightarrow A_1 = CV$$

General solution of full eq.



$$Q(t) = CV + A \exp\left(-\frac{t}{RC}\right)$$

$$Q(0) = 0 \Rightarrow CV + A = 0 \Rightarrow A = -CV$$

$$Q(t) = CV \left[ 1 - \exp\left(-\frac{t}{RC}\right) \right]$$

$$i(t) = +\frac{V}{R} \exp\left(-\frac{t}{RC}\right)$$

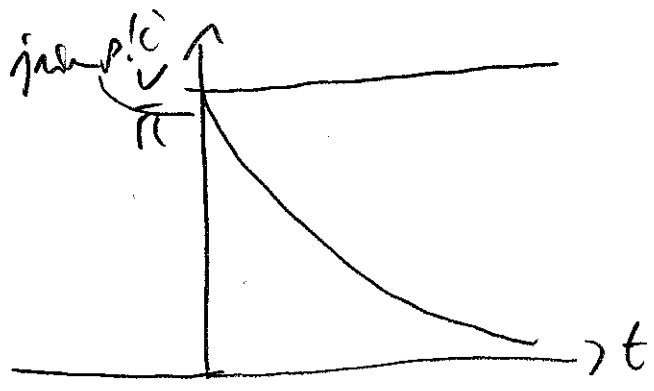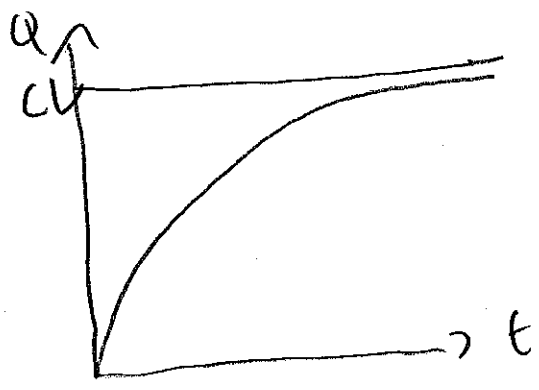For first moment circuit behaves as if there were no capacitor.




Long-time limit: goes to steady state, i.e., no current and  $Q = CV$ , i.e., voltage of the capacitor becomes the voltage of Battery.

Limit  $R \rightarrow 0$

Since  $t \gg RC$ , the approx holds simply correct, and we have immediately the steady-state limit. The sudden jumps in  $Q$  (or the current in the case of finite resistance) is due to the inductance of the circuit's self inductance.

# Dissipation of a capacitor

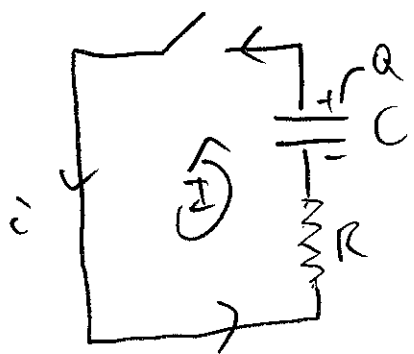

$$Q(0) = Q_0 > 0$$

$$I: RCi - \frac{Q}{C} = 0$$

$$i = -\dot{Q}$$

↑ current runs away from + plate!

$$\Rightarrow \dot{Q} + \frac{Q}{RC} = 0$$

no more work done from a battery

$$\Rightarrow Q(t) = A \exp\left(-\frac{t}{RC}\right)$$

initial condition:  $Q(0) = Q_0 = A$

$$Q(t) = Q_0 \exp\left(-\frac{t}{RC}\right)$$

$$i(t) = -\dot{Q}(t) = \frac{Q_0}{RC} \exp\left(-\frac{t}{RC}\right)$$

Energy stored in capacitor dissipates as heat in resistor

$$P = Ri^2 = \frac{Q_0^2}{RC^2} \exp\left(-\frac{2t}{RC}\right)$$

$$E = \int_0^{\infty} dt P(t) = \frac{Q_0^2}{RC^2} \int_0^{\infty} \exp\left(-\frac{2t}{RC}\right) dt$$

$$= -\frac{Q_0^2}{2C} \exp\left(-\frac{2t}{RC}\right) \Big|_0^{\infty} = \frac{Q_0^2}{2C}$$


$$E = \frac{Q_0}{2\epsilon}$$

has been shown in the electric field before we closed the switch. Thus we have already found out how it is on the course in a different way.

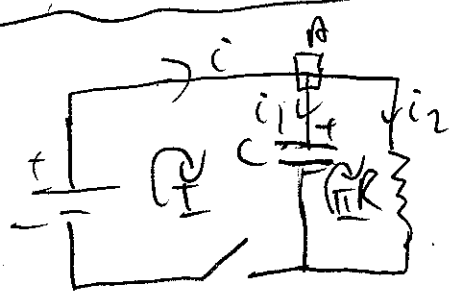(b) DC parallel circuit

Initial conditions

$$\begin{cases} Q(0) = 0 \\ \text{all currents } 0 \\ \text{at } t=0 \end{cases}$$



$$\begin{aligned} \text{A: } i &= i_1 + i_2 \\ \text{I: } -V + \frac{Q}{C} &= 0 \\ \text{II: } -\frac{Q}{C} + Ri_2 &= 0 \end{aligned}$$

$$i_1 = \dot{Q}$$


$$\text{I} - \text{II} \Rightarrow -V + Ri_2 = 0 \Rightarrow \boxed{i_2 = \frac{V}{R}}$$

$$\text{I} \Rightarrow \frac{Q}{C} = V = \text{const} \Rightarrow \boxed{Q = CV}$$

$$i_1 = \dot{Q} = 0 \Rightarrow i = i_2 = \frac{V}{R}$$

The currents and the charges jump to their steady-state values. Reason: Negligence of R in C branch and of L in both loops.

(c) DC series

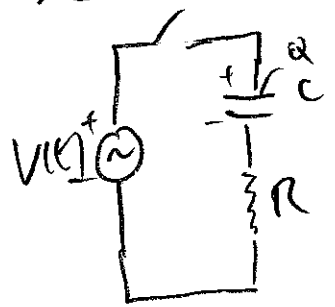

Same eqs as in (a) but with

$$V(t) = V_0 \cos(\omega t)$$

$$\Rightarrow \dot{Q} + \frac{1}{RC} Q = \frac{V_0}{R} \cos(\omega t)$$

Need only to find new particular solution of  
Unknown. eq.

"Ansatz of type of right-hand side of equation"

$$Q = A_1 \cos(\omega t) + B_1 \sin(\omega t)$$

$$\dot{Q} = -A_1 \omega \sin(\omega t) + B_1 \omega \cos(\omega t)$$

$$-A_1 \omega \sin \omega t + B_1 \omega \cos(\omega t) + \frac{1}{RC} [A_1 \cos(\omega t) + B_1 \sin(\omega t)] = \frac{V_0}{R} \cos(\omega t)$$

$$\Rightarrow \frac{A_1}{RC} + B_1 \omega = \frac{V_0}{R}$$

$$-A_1 \omega + \frac{B_1}{RC} = 0 \Rightarrow B_1 = A_1 RC \omega$$

$$\Rightarrow \frac{A_1}{RC} + A_1 RC \omega^2 = \frac{V_0}{R}$$

$$A_1 \left( \frac{1 + \pi^2 \omega^2}{RC} \right) = \frac{V_0}{R}$$

$$\Rightarrow A_1 = \frac{C V_0}{1 + (RC\omega)^2}$$

$$B_1 = \frac{RC^2 \omega V_0}{1 + (RC\omega)^2}$$

Solution

$$Q(t) = A \exp\left(-\frac{t}{RC}\right) + A_1 \cos(\omega t) + B_1$$

Initial conditions

$$Q(0) = A + A_1 = 0 \Rightarrow A = -A_1$$

$$Q(t) = \frac{C V_0}{1 + (RC\omega)^2} \left[ \cos(\omega t) - \exp\left(-\frac{t}{RC}\right) \right]$$

$$+ \frac{RC^2 \omega V_0}{1 + (RC\omega)^2} \sin(\omega t)$$

$$\dot{Q}(t) = \dot{Q}(t) = C \frac{V_0}{1 + (RC\omega)^2} \left[ -\omega \sin(\omega t) + \frac{1}{RC} \exp\left(-\frac{t}{RC}\right) \right]$$

$$+ \frac{RC^2 \omega^2 V_0}{1 + (RC\omega)^2} \cos(\omega t)$$

Long time limit ("stationary state") ( $t \gg RC$ )

$$i_{\infty}(t) = -A_1 \omega \sin(\omega t) + B_1 \omega \cos(\omega t)$$

Amplitude and phase shift

$$i_{\infty}(t) = A_{i\infty} \cos(\omega t + \phi_0)$$

$$= A_{i\infty} [\cos(\omega t) \cos \phi_0 - \sin(\omega t) \sin \phi_0]$$

$$\Rightarrow A_{i\infty} \cos \phi_0 = B_1 \omega$$

$$A_{i\infty} \sin \phi_0 = +A_1 \omega$$

$$A_{\text{in}}^2 = (A_1^2 + B_1^2) \omega^2$$

$$= \frac{\omega^2 V_0^2}{[1 + (RC\omega)^2]^2} (C^2 + R^2 C^3 \omega^2)$$

$$= \frac{\omega^2 V_0^2 C^2}{[1 + (RC\omega)^2]^2} [1 + \cancel{(RC\omega)^2}]$$

$$\Rightarrow A_{\text{in}} = \frac{\omega C}{\sqrt{1 + (RC\omega)^2}} V_0$$

$$\phi_0 = \text{Sign}(A_1) \arcsin\left(\frac{V_{B_1}}{A_{\text{in}}}\right) = + \arcsin\left(\frac{RC\omega^2 C^2}{\omega C \sqrt{1 + (RC\omega)^2}}\right)$$

$$\phi_0 = \arcsin\left(\frac{RC\omega}{\sqrt{1 + (RC\omega)^2}}\right)$$

For  $\omega \rightarrow 0$  we are in the static limit and



$$A_{\text{in}}(\omega=0) = 0 \quad (\text{no current through resistor})$$

$$\phi_0 \rightarrow \frac{\pi}{2} \quad (\text{no physical meaning since current} = 0)$$

For high-frequency limit  $\omega \rightarrow \infty$

$$A_{\text{in}}(\omega \rightarrow \infty) = \frac{V_0}{R} \quad (\text{capacitance becomes negligible})$$
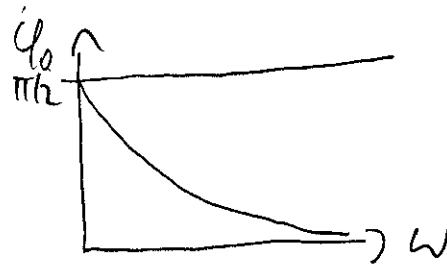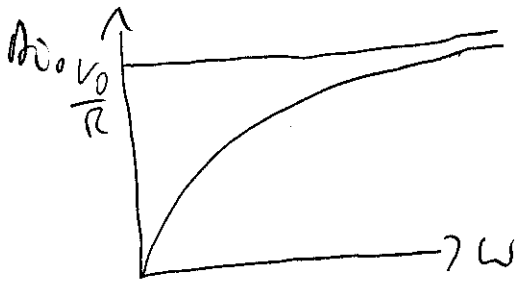
$$\phi_0(\omega \rightarrow \infty) = 0 \quad (\text{no phase shift})$$




For  $R \rightarrow 0$

$$A_{i\omega} |_{R \rightarrow 0} = \omega C V_0$$

$$\phi_0 = \frac{\pi}{2}$$

$\phi_0$  is always positive  $\Rightarrow$  current advances voltage in stationary limit.

RLC - parallel circuit

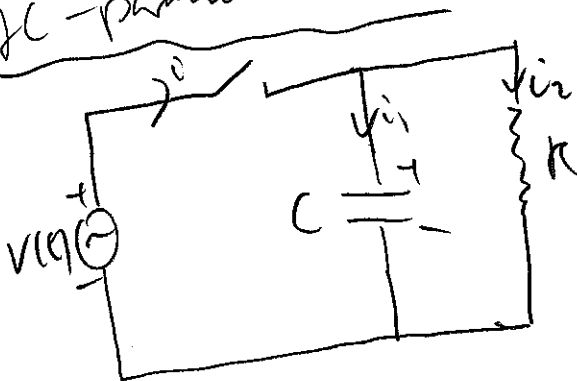

$Q(0) = 0$   
 $t=0 \Rightarrow$  all currents 0  
 $v(t) = V_0 \cos(\omega t)$

From (b)

(I)  $Q = V_0 \cos(\omega t)$

(II)  $i_2 = \frac{V_0}{R} \cos(\omega t)$

$i_1 = \dot{Q} = -V_0 \omega C \sin(\omega t)$

$i = i_1 + i_2 = V_0 \left[ \frac{1}{R} \cos(\omega t) - \omega C \sin(\omega t) \right]$

Jumps in  $i$  are known by to stationary state (same reasons as discussed in case (b)).



Current through resistor

$$A_{oi2} = \frac{V_0}{R} \quad | \quad \phi_{oi2} = 0$$

Current through capacitor

$$i_1 = -V_0 \omega C \sin(\omega t) = V_0 \omega C \cos(\omega t + \frac{\pi}{2})$$

$$\Rightarrow A_{oi1} = V_0 \omega C$$

$$\phi_{oi1} = \frac{\pi}{2}$$

Total current

$$i(t) = V_0 \left[ \frac{1}{R} \cos(\omega t) - \omega C \sin(\omega t) \right]$$

$$\Rightarrow A_{oi}^2 = \left( \frac{1}{R^2} + \omega^2 C^2 \right) V_0^2 = \frac{1 + (RC\omega)^2}{R^2} V_0^2$$

$$\Rightarrow A_{oi} = \frac{\sqrt{1 + (RC\omega)^2}}{R} V_0$$

$$\phi_{oi} = + \arccos\left(\frac{1}{R A_{oi}}\right) = \arccos\left(\frac{1}{\sqrt{1 + (RC\omega)^2}}\right)$$

$$\omega \rightarrow 0 \Rightarrow A_{oi} \rightarrow \frac{V_0}{R}$$

$$\Rightarrow \phi_{oi} \rightarrow 0$$

$$\omega \rightarrow \infty \Rightarrow A_{oi} \xrightarrow{\omega \rightarrow \infty} V_0 C \omega$$

$$\Rightarrow \phi_{oi} \rightarrow \frac{\pi}{2}$$

