

Problems - Chapter VI


(1) $C = \frac{A \epsilon_0}{d} \Rightarrow A = \frac{C \cdot d}{\epsilon_0} = \frac{1}{4\pi \epsilon_0} 4\pi C d$
 With $C = 1 \text{ F}$ and $d = 1 \text{ cm} = 10^{-2} \text{ m}$: $A = 1.13 \cdot 10^9 \text{ m}^2$

(2) $C = \frac{A \epsilon_0}{d}$; $\epsilon_0 \approx 8.84 \cdot 10^{-12} \frac{\text{F}}{\text{m}}$
 $C = 2.65 \cdot 10^{-10} \text{ F} = 265 \text{ pF}$

$Q = CV = 3.18 \cdot 10^{-9} \text{ C}$ on the plate connected to the + terminal ($-3.18 \cdot 10^{-9} \text{ C}$ on the other plate)
 When the battery is disconnected these charges stay on the plates. Moving the plates together

$C' = \frac{A \epsilon_0}{d'} = C \frac{d}{d'} = 3C = 796 \text{ pF}$

The voltage is
 $V' = \frac{Q}{C'} = \frac{Q}{C} \frac{C}{C'} = \frac{V}{3} = 4 \text{ V}$

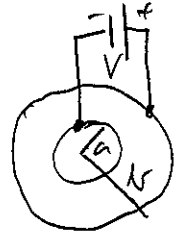(3)  The field between the plates is a constant field (see last week's problems and exercises)

$\Rightarrow V(r) = -\frac{Q}{4\pi \epsilon_0} \frac{1}{r}$

The voltage here is

$V = V(b) - V(a) = \frac{Q}{4\pi \epsilon_0} \left(\frac{1}{a} - \frac{1}{b} \right)$ (> 0 as it should be)

Then
 $C = \frac{Q}{V} = \frac{4\pi \epsilon_0}{\frac{1}{a} - \frac{1}{b}} = \frac{4\pi \epsilon_0 a b}{b - a}$

(14) $C_{\text{simple plate}} = \epsilon_0 \epsilon_r \frac{A}{d}$

For a simple plate this doesn't work, because we made the assumption that $d \ll \sqrt{A}$. It would be very complicated to solve the boundary-value problem for a finite simple plate!

(15)



$$C_{\text{total}} = \frac{C_1 C_2}{C_1 + C_2} \quad (\text{Capacitors in series})$$

and $C_1 = \frac{\epsilon_0 A}{b}$; $C_2 = \frac{\epsilon_0 A}{b-d}$

$$C_{\text{total}} = \frac{(\epsilon_0 A)^2}{b(b-d) \left(\frac{1}{b} + \frac{1}{b-d} \right)}$$

$$= \frac{\epsilon_0 A}{b-d + b} = \frac{\epsilon_0 A}{b-d}$$

It doesn't matter, where we insert the plate!

Exercises - Chpt. VI

$$(1) C = \frac{Q}{V} = \frac{0.1 \text{ C}}{100 \text{ V}} = 10^{-3} \text{ F} (= 1 \text{ mF})$$

$$C = \frac{\epsilon_0 A}{d} \Rightarrow A = \frac{C d}{\epsilon_0} = \frac{4\pi C d}{4\pi \epsilon_0} = 1.13 \cdot 10^5 \text{ m}^2$$

$$(2) C_{\text{total}} = \frac{C_1 C_2}{C_1 + C_2}$$

Set $C_1 + C_2 = C_3 = \text{const.}$ Then we have

$$C_{\text{total}} = \frac{C_1 (C_3 - C_1)}{C_3}$$

look for extreme:

$$\frac{dC_{\text{total}}}{dC_1} = -\frac{1}{C_3} (C_3 - 2C_1) \stackrel{!}{=} 0 \Rightarrow C_1 = \frac{C_3}{2} = C_2$$

$$\frac{d^2 C_{\text{total}}}{dC_1^2} = -\frac{2}{C_3} < 0 \Rightarrow \text{maximum}$$


minimum for $C_1 = 0$ or $C_2 = 0$

$$(c) C_{\text{tot}} = C_1 + C_2$$

\Rightarrow it's always the same, since $C_{\text{tot}} = C_1 + C_2$ is fixed.


(3) Find all combinations

(2)

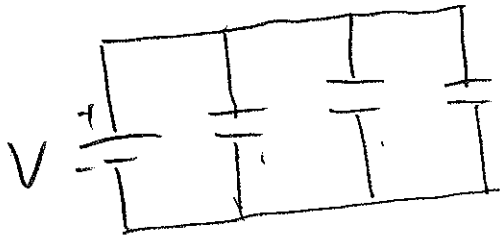

$$C_{\text{tot}} = C_1 + C_2 + C_3 = 14 \mu\text{F}$$

order doesn't play any role

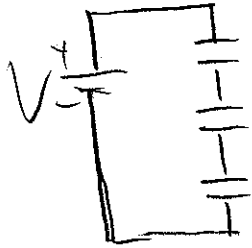


$$\frac{1}{C_{\text{tot}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$= \left(\frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) \frac{1}{\mu\text{F}}$$


$$= \frac{7}{8} \frac{1}{\mu\text{F}} \Rightarrow C_{\text{tot}} = \frac{8}{7} \mu\text{F}$$

order doesn't play a role

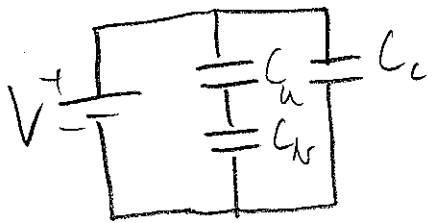

$$C_{\text{tot}} = \frac{C_a C_b}{C_a + C_b} + C_c$$

a	b	c	total
1	2	3	$\frac{28}{3} \mu\text{F}$
1	3	2	$\frac{28}{5} \mu\text{F}$
2	3	1	$\frac{14}{3} \mu\text{F}$

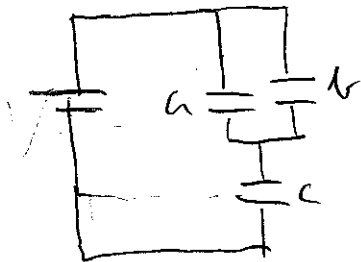

$$\frac{1}{C_{\text{tot}}} = \frac{1}{C_a + C_b} + \frac{1}{C_c}$$

a	b	c	total
1	2	3	$24 \frac{1}{7} \mu\text{F}$
1	3	2	$10 \frac{1}{7} \mu\text{F}$
2	3	1	$12 \frac{1}{7} \mu\text{F}$


(4) A series of two spherical capacitors with $C_1 = 4\pi\epsilon_0 \frac{ab}{b-a}$ and $C_2 = 4\pi\epsilon_0 \frac{c(b+r)}{c-b-r}$ (3)

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{4\pi\epsilon_0} \left(\frac{1}{a} - \frac{1}{b} + \frac{1}{b+r} - \frac{1}{c} \right)$$

$$= \frac{1}{4\pi\epsilon_0} \left(\frac{b(b+r)c - a(b+r)c + abc - ab(b+r)}{ab(b+r)c} \right)$$

$$= \frac{1}{4\pi\epsilon_0} \left(\frac{b^2c + bct - abc - act + abc - ab^2 - abt}{ab(b+r)c} \right)$$

$$C = \frac{4\pi\epsilon_0 abc(b+r)}{b^2c + bct - act - ab^2 - abt}$$

~~(5) (a) $Q_1 = VC_1, Q_2 = VC_2 \Rightarrow Q = Q_1 + Q_2 = V(C_1 + C_2)$
 The (approx $C_1 > C_2$) The over the total capacity C

 $C = \frac{C_1 C_2}{C_1 + C_2}$
 is the charge $Q_1 = Q_2 = Q = (C_1 + C_2)V$
 The new voltage $V = \frac{Q}{C} = Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = V \left(1 - \frac{C_2}{C_1} + \frac{C_1}{C_2} + 1 \right)$
 $= V \left(\frac{C_1 + C_2}{C} \right)$~~

5.87 $C_1 > C_2$



Total charge on the system is

$$Q = (C_1 - C_2) V$$

The total voltage difference is 0

$$\Rightarrow \frac{Q_1}{C_1} - \frac{Q_2}{C_2} = 0 \Rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow Q_2 = \frac{C_2}{C_1} Q_1$$

$$\text{but } Q_1 + Q_2 = Q \Rightarrow Q_1 + \frac{C_2}{C_1} Q_1 = Q$$

$$\Rightarrow Q_1 = \frac{Q}{1 + \frac{C_2}{C_1}} = \frac{Q C_1}{C_1 + C_2} = \frac{C_1 (C_1 - C_2) V}{C_1 + C_2}$$

$$\Rightarrow Q_2 = \frac{Q C_2}{C_1 + C_2} = \frac{C_2 (C_1 - C_2) V}{C_1 + C_2}$$